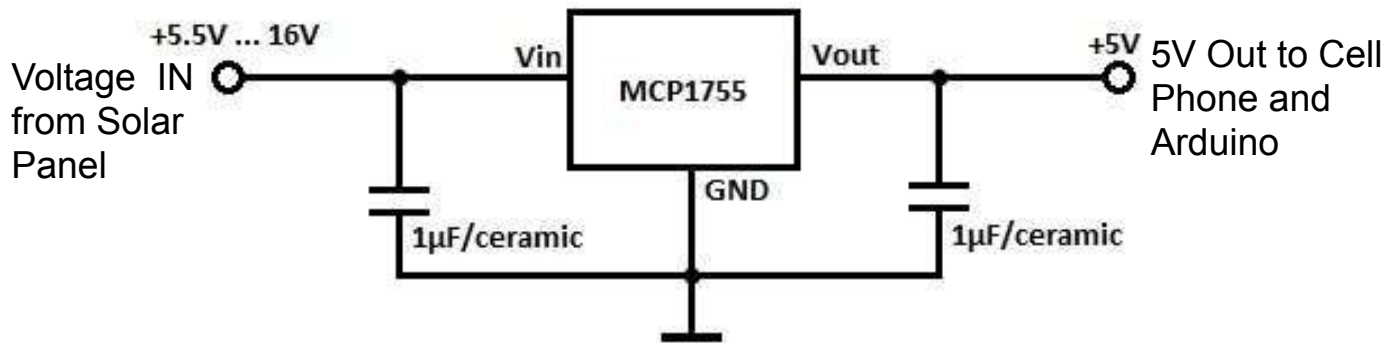



# Electronic Designs

## 5V Regulator to Cell Phone and Arduino:



## Voltage reduction to Arduino:

To Arduino Pin A0

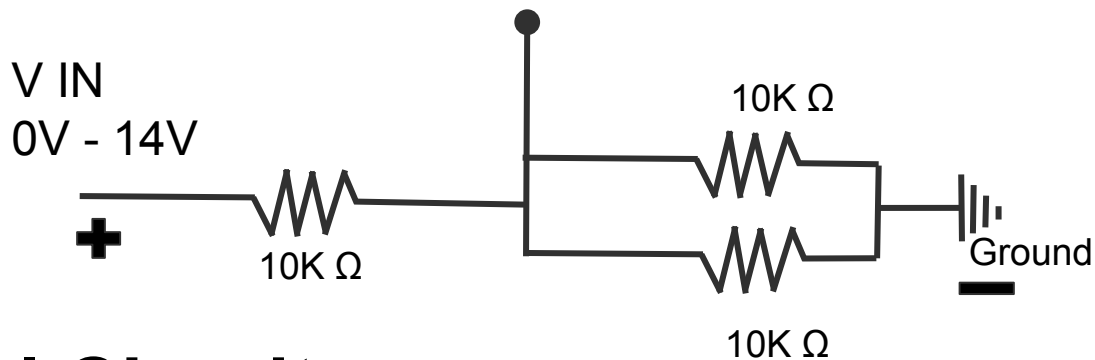

## Final Circuitry:

VIN from Solar Panel

LCD Circuitry

Voltage Regulator

5V OUT to Cell Phone and Arduino

Voltage Reduction

to Arduino

